

Roll No.

24324

**B. Tech 6th Semester (CSE)
Examination – May, 2018**

DIGITAL SYSTEM DESIGN

Paper : EE-310-F

Time : Three Hours]

[Maximum Marks : 100

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt *five* question in all, selecting *one* question from each Section. Question No. 1 is *compulsory*. All questions carry equal marks.

1. (i) Define data types and data objects. 5
- (ii) Differentiate between concurrent and sequential statement. 5
- (iii) Explain why simulation is required. 5
- (iv) What is GAL ? 5

SECTION – A

2. (a) Discuss different types of delay models used in VHDL. 15
- (b) Explain different types of operator used in VHDL. 5

3. What is overloading ? Explain different types of overloading used in VHDL with suitable examples in detail. 20

SECTION - B

4. Explain the following : 20
- (i) Procedures
 - (ii) Package and Library
 - (iii) Component declaration and instantiation
 - (iv) Generics
5. (a) Write VHDL code for 4:1 Mux using
- (i) Case Statement
 - (ii) If Then Else statement 10
- (b) What is the difference between function and procedures ? Explain with the help of examples. 10

SECTION - C

6. (a) Write VHDL code for design of an Mod-10 asynchronous counter. 10
- (b) Implement the following Boolean function $F = B + CD + AE$ using :
- (i) Nand- Nand logic
 - (ii) Nor-Nor logic 10

7. Write VHDL code for the following sequential circuit : 20

- (i) SISO shift register
- (ii) 1:16 Demux

SECTION - D

8. Write short note on : 20

- (i) PEEL
- (ii) FPGA
- (iii) CPLD

9. (a) Implement $F(A,B,C,D) = \Sigma (2,4,6,7)$ using PAL. 10

(b) Draw and discuss in detail the architecture of simple micro computer. 10
