

B. Tech. 5th Semester (F) Scheme (EEE)

Examination, December-2018

ANALOG ELECTRONIC CIRCUIT

Paper-EE-305-F

Time allowed : 3 hours]

[Maximum marks : 100

Note : First question is compulsory. Attempt five questions in all, selecting one question from each section.

1. (a) Explain the effects of coupling and bypass capacitor in a circuit.
- (b) What is an oscillator ? How does it differ from an amplifier ?
- (c) Distinguish between Class -A, Class-B and Class-C operation of amplifiers.
- (d) Differentiate between linear and non linear applications of operational amplifiers. 5×4

Section-A

2. Define the lower cut-off frequency and upper cut-off frequency. Derive expression for these frequencies in terms of circuit components. Draw the frequency response curve of an R-C coupled amplifier. 20

(2)

24227

3. (a) Differentiate between positive and negative feedback. How does negative feedback modify the gain of an amplifier? 10
- (b) What is the effect of unbypassed emitter lead resistance R_E on the gain of an amplifier? 10

Section-B

4. (a) What are the Barkhausen condition of oscillations in electronic systems? What are the factors which affect the frequency stability of an oscillator? 10
- (b) Explain how oscillations are initiated and sustained in an oscillator. Draw the ckt diagram of an R-C phase shift oscillator and briefly explain the principle of operation. 10
5. Enumerate the advantages of R-C oscillators. Explain the working of an R-C phase shift oscillator and find the expression for its frequency of oscillation. Find the limit on the gain of amplifier used in this oscillator. 20

Section-C

6. (a) Explain how the position of Q-point varies in case of Class-A, B and C operation. 10
- (b) Draw the circuit of a push-pull amplifier and

(3)

24227

7. Draw the circuit diagram of an inverting amplifier using op-amp and derive the expression for its voltage gain. Explain the significance of virtual ground. Define CMRR of a differential amplifier. Realize a differentiator using op-amp. 10

Section-D

8. Write note on –
- (i) Bridge amplifier
 - (ii) Current to voltage converter
 - (iii) Scale changer
 - (iv) Phase shifter 20
9. Write notes on :
- (i) Comparators
 - (ii) Logarithmic Amplifier
 - (iii) APC
 - (iv) Waveform Generator. 20