

Roll No.

24025

**B. Tech 3rd Sem. (EEE)
Examination – December , 2018**

NETWORK THEORY

Paper : EE-203-F

Time : Three Hours] [Maximum Marks : 100

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt any *five* questions, *one* question from each Section. Question No. 1 is *compulsory*.

1. Explain the following terms in network theory :

5 × 4 = 20

- (i) Mesh analysis
- (ii) KVL & KCL
- (iii) Current division rule
- (iv) Laplace transform
- (v) Transfer function

SECTION – A

2. (a) State and prove Theverin's theorem. 10

24025-4,000-(P-3)(Q-9)(18)

P. T. O.


- (b) Obtain Z parameter of the circuit shown : 10




3. (a) Derive the condition for reciprocity & symmetry for ABCD parameter. 10
 (b) Derive the relationship between Z & ABCD parameters. 10

SECTION - B

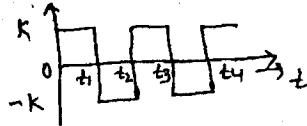4. (a) What is the Laplace transform of waveform shown ? 10



- (b) Synthesize the waveform : 10

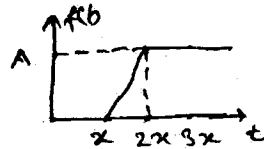

5. (a) In a series LC circuit of 50 dc is applied at $t = 0$. Find the voltage across the capacitor at $t = \infty$. Assume zero initial condition in the circuit elements. 10
 (b) Obtain the pole zero diagram of the given function and obtain the time domain response : 10

$$I(S) = \frac{2S}{(S+1)(S^2 + 2S + 4)}$$

SECTION - C

6. (a) A function is given by : 10

$$Z(S) = \frac{S^3 + 5S^2 + 9S + 3}{S^3 + 4S^2 + 7S + 9}$$

Find the positive realness of the function.

- (b) Test whether the following functions are Hurwitz or not : 10

$$S^4 + 3S^2 + 2$$

7. The driving point impedance of a network is given by : 20

$$Z(S) = \frac{8(S^2 + 1)(S^2 + 3)}{S(S^2 + 2)(S^2 + 4)}$$

Realise the network in Foster I, II.

SECTION - D

8. (a) Synthesize the following function using 1Ω termination $Z_{21}(S) = 1/S^3 + 3S^2 + 3S + 2$. 10
 (b) Explain tie-set, cut set in graph theory. 10
 9. (a) Explain different properties of transfer function. 10
 (b) Derive step & impulse response of a series RL circuit. 10