

Roll No.

21276

**B. Sc. (Physics) (Hons.) 2nd Semester
Examination – May, 2019**

**LINEAR AND DIGITAL INTEGRATED CIRCUITS &
INSTRUMENTS-II**

Paper : Phy-206

*Time : Three hours] [Maximum Marks : 40
Before answering the questions, candidates should ensure that
they have been supplied the correct and complete question
paper. No complaint in this regard, will be entertained after
examination.*

*Note : A student has to attempt five questions in all,
selecting at least two questions from each Unit.*

UNIT – I

1. Answer the following questions briefly : $2 \times 4 = 8$
- (a) Explain the race-around condition in flip-flops.
 - (b) Define the term accuracy and resolution for analog
to digital converter.

P. T. O.

- (c) Explain serial-in-parallel-out(SIPO) shift register.
- (d) What are sequential circuits ? Explain with suitable examples ?
2. (a) Explain the working of master-slave JK flip-flop with suitable diagrams. 5
- (b) Derive characteristic equations of SR & JK flip-flop. 3
3. (a) Compare synchronous and asynchronous counters. 3
- (b) Design a MOD 6 synchronous counter. 5
4. A weighted resistor D/A converter has $n = 8$ bit, the reference voltage $V_R = 10$ V, the resistance $R = 12$ K Ω (Kilo ohm) and feedback resistance of the op-amp $R_f = 6$ K Ω . Calculate : 8
- (a) The output voltage V_o corresponding to LSB.
- (b) The output voltage V_o corresponding to MSB.
- (c) Maximum value output voltage V_o .

(2)

- (d) Nominal full scale output voltage V_o .
- (e) Resolution.
- (f) The output voltage V_o corresponding to bit input 10101100.

UNIT - II

5. Explain in detail the working of full wave bridge rectifier with suitable waveform diagrams. Also derive the expression or its ripple factor.
6. What are filters ? Explain the working of L & C filter in detail.
7. (a) Draw and explain the block diagram of CRO. Explain how frequency is measured using CRO ?
- (b) Explain the working of time base generator with suitable diagrams. 3
8. (a) Draw the pin diagram and explain the function of various pins of IC 555 timer. 4
- (b) Explain the working of IC 555 timer as a multivibrator. 4

(3)