

91031

B.Sc. 1st Semester (Hons) Examination,

November-2014

PHYSICS

Paper-Phy-106

Linear Digital Integrated Circuits and Instrumentation-I

Time allowed : 3 hours]

[Maximum marks : 40

Note : Attempt five questions in all, selecting at least two questions from each unit.

Unit-I

1. (a) List the difference between thick and thin film IC's. 4
- (b) Differentiate between Linear Integrated circuits and Digital Integrated circuits. 4
2. (a) What is an OP-AMP ? Draw and explain the block diagram of OP-AMP. 4
- (b) Why are open loop OP-AMP configurations not used in linear applications ? 2
- (c) Write four characteristics of OP-AMP (ideal). 2
3. (a) Calculate the output voltage of a OP-AMP summer for the following set of input voltages and resistors
 $V_1 = 1 \text{ volt}, V_2 = 2 \text{ volt}, V_3 = 3 \text{ volt}$
 $R_1 = 500 \text{ k}\Omega, R_2 = 1\text{M}\Omega, R_3 = 1\text{M}\Omega$ and
 $R_F = 1\text{M}\Omega$ 4
- (b) Write a note on zero crossing detector. 4

4. (a) What is the difference between an oscillator and multivibrator ? Draw the circuit of bistable multivibrator and find the expression for collector swing of one transistor used in the multivibrator. 6
- (b) How can a operational amplifier be used as a comparator ? 2

Unit-II

5. (a) How the decimal fraction numbers are converted to binary numbers ? Explain. 3
- (b) Convert hexadecimal number 2 BAFC to binary and then to octal. 3
- (c) What do you understand by floating point representation of binary numbers ? 2
6. (a) What is the difference between the ordinary algebra and Boolean algebra ? 2
- (b) Explain how AND, OR, NOT gates can be realized using NOR gates alone. 4
- (c) Draw a truth table of a Boolean function $F = \overline{A} \cdot B + C$. 2
7. (a) What is memory unit ? Explain with block diagram the concept of memory using registers connected to memory unit. 4
- (b) Explain the working of Encoder with a neat and clean diagram. 4

8. (a) Implement a half Adder circuit using NAND gate only. 3
- (b) Draw the diagram of a full subtractor and explain its working. 3
- (c) Obtain 2's complement of 16 bit binary number 0111100011001100 by two methods. 2