

Library  
4E2086

Roll No. : \_\_\_\_\_

Total Printed Pages : 3

4E2086

B. Tech. (Sem. IV) (Back/Old Scheme) Examination, June/July - 2011

Electronics & Comm.

4EI2 Analog Electronics

Common for EC & EIC

Time : 3 Hours]

[Total Marks : 80

[Min. Passing Marks : 24

Attempt any **five** questions. Selecting **one** question from each unit.

All questions are carry **equal** marks.

Schematic diagrams must be shown wherever necessary. Any data you feel missing any suitably be assumed and stated clearly).

Units of quantities used/calculated must be stated clearly

Use of following supporting material is permitted during examination.  
(Mentioned in form No. 205)

1. \_\_\_\_\_ Nil

2. \_\_\_\_\_ Nil

### UNIT - I

- 1 (a) Draw the block diagram of a negative feedback amplifier. Derive an expression for the voltage gain of an amplifier of gain A when subjected to negative feedback with a feedback fraction B.

8

- (b) State the merits and demerits of negative feedback amplifier.

8

- 2 (a) Discuss the effect of negative feedback on :

- (i) Distortion
- (ii) Output impedance
- (iii) Input impedance

- (b) An amplifier with current feedback has the following specifications :

$$h_{fe} = 100\Omega; h_{ie} = 2000\Omega, R_1 = 15000\Omega$$

$$R_2 = 5600\Omega, R_e = 100\Omega \text{ and } R_L = 470\Omega$$

Calculate the values of voltage gain and input resistance of the amplifier with and without feedback.

8

4E2086]



1

[Contd...

## UNIT - II

- 3 (a) Find an expression for the frequency of oscillations and condition for sustaining the oscillation in tuned collector oscillator. 8
- (b) Describe Hartley oscillator circuit and explain its action. 8
- 4 (a) Sketch the circuit of schmitt trigger and explain its operation. 8
- (b) What is a monostable multivibrator ? Explain its working with the help of neat waveform ? 8

## UNIT - III

- 5 Draw the circuit diagram of emitter follower at high frequencies. Also explain its behaviour at high frequencies with necessary expression and parameter. 16
- 6 Determine gain bandwidth product, unity gain frequency using hybrid  $\pi$  model for CE configuration. 16

## UNIT - IV

- 7 (a) Sketch 2 - input XOR function using static CMOS circuit technique, assume complementary signals are not available. 8
- (b) Explain with neat diagram the working of a totem pole two input TTL NAND gate. 8



- 8 (a) Explain the parameters used to characterize logic families. 8
- (b) Write brief notes on ECL and RTL logic families. 8

### UNIT - V

- 9 (a) Draw the circuit diagram of a push - pull amplifier. Explain its operation. Discuss its advantages and disadvantages. 3+3+2
- (b) Show that maximum collector efficiency of class A transformer coupled power amplifier is 50%. 8
- 10 (a) What do you understand by class A, B and C power amplifiers ? 8
- (b) Define and explain the following terms as applied to power amplifiers :  
(i) Collector efficiency  
(ii) Power dissipation capability  
(iii) Overall gain. 3+3+2
- 

