

5E3253-R

Roll No. : _____

Total Printed Pages : 3

5E3253-R

B. Tech. (Sem. V) (Main) Examination, December - 2011
5CS2 Digital Logic Design

Time : 3 Hours]

[Maximum Marks : 80]

[Min. Passing Marks : 24

Instructions to Candidates :

Attempt any five questions selecting one question from each unit. All questions carry equal marks. Schematic diagrams must be shown wherever necessary. Any data you feel missing suitably be assumed and stated clearly. Units of quantities used/calculated must be stated clearly.

Use of following supporting material is permitted during examination.
(Mentioned in form No. 205)

1. NIL

2. NIL

UNIT - I

- 1 (a) Why we use hardware description language and explain what is use in digital logic design ? 8
- (b) Explain different data type in HDL modeling. 8

OR

- 1 (a) Explain different type of modeling in VHDL with example. 8
- (b) Write a program of Ripple Carry adder in VHDL language. 8

UNIT - II

- 2 (a) Explain different kinds of subprogram with examples. 8
- (b) Write a behavioural description of a D-flipflop. 8

OR



- 2 (a) What is difference of Generate and concurrent statement ?
Explain with suitable example.

8

- (b) What is simulation and synthesis process in VHDL ?

8

UNIT - III

- 3 (a) Describe the steps of synchronous sequential circuit with suitable example.

8

- (b) Explain Moore and Melay machine and describe the clock skew.

8

OR

- 3 Discuss the concept and working principle of following :
(any four)

(i) ROM

(ii) FPGA

(iii) PLA

(iv) PLD

(v) Setup time and Hold time.

16

UNIT - IV

- 4 (a) What do you mean by event driven circuit ?

8

- (b) Explain design procedure of asynchronous circuits.

8

OR



- 4 (a) What is races and what is process of race free assignment ? 8
- (b) Describe all type of Hazard in combination networks. 8

UNIT - V

- 5 Why we use FPGA kits and explain logic elements and programmability. 16

OR

- 5 Write short notes on : (any two)
- (a) SRAM
 - (b) Flash Memory
 - (c) Lookup Table Technology.
- 16